

Unit 4.3: Fourier Transforms for Circuit and LTI Systems Analysis

Contents

- Colophon
- Agenda
- The System Function
- Examples
- Solutions

Colophon

An annotatable worksheet for this presentation is available as [Worksheet 7](#).

- The source code for this page is [fourier_transform/3/ft3.md](#).
- You can view the notes for this presentation as a webpage ([Unit 4.3: Fourier Transforms for Circuit and LTI Systems Analysis](#)).
- This page is downloadable as a [PDF](#) file.

In this section we will apply what we have learned about Fourier transforms to some typical circuit problems. After a short introduction, the body of this chapter will form the basis of an examples class.

Agenda

- The system function
- Examples

The System Function

System response from system impulse response

Recall that the convolution integral of a system with impulse response $h(t)$ and input $u(t)$ is

$$h(t) * u(t) = \int_{-\infty}^{\infty} h(t - \tau)u(\tau) d\tau.$$

We let

$$g(t) = h(t) * u(t)$$

Then by the time convolution property

$$h(t) * u(t) = g(t) \Leftrightarrow G(\omega) = H(\omega) \cdot U(\omega)$$

The System Function

We call $H(\omega)$ the *system function*.

We note that the system function $H(\omega)$ and the impulse response $h(t)$ form the Fourier transform pair

$$h(t) \Leftrightarrow H(\omega)$$

Obtaining system response


If we know the impulse response $h(t)$, we can compute the system response $g(t)$ of any input $u(t)$ by multiplying the Fourier transforms of $H(\omega)$ and $U(\omega)$ to obtain $G(\omega)$. Then we take the inverse Fourier transform of $G(\omega)$ to obtain the response $g(t)$.

1. Transform $h(t) \rightarrow H(\omega)$
2. Transform $u(t) \rightarrow U(\omega)$
3. Compute $G(\omega) = H(\omega) \cdot U(\omega)$
4. Find $\mathcal{F}^{-1}\{G(\omega)\} \rightarrow g(t)$

Examples

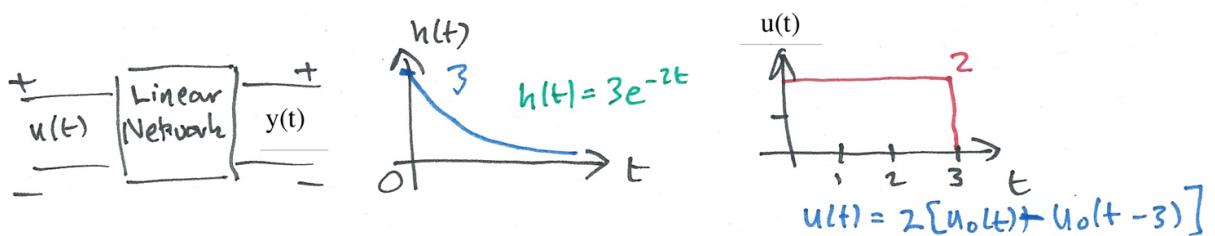Example 1

Karris example 8.8: for the linear network shown below, the impulse response is $h(t) = 3e^{-2t}$. Use the Fourier transform to compute the response $y(t)$ when the input $u(t) = 2[u_0(t) - u_0(t - 3)]$. Verify the result with MATLAB.



Solution to example 1

Matlab verification of example 1

```
syms t w  
U1 = fourier(2*heaviside(t),t,w)
```

```
U1 =
```

```
2*pi*dirac(w) - 2i/w
```

```
H = fourier(3*exp(-2*t)*heaviside(t),t,w)
```

```
H =
```

```
3/(2 + w*1i)
```

```
Y1=simplify(H*U1)
```

```
Y1 =
```

```
3*pi*dirac(w) - 6i/(w*(2 + w*1i))
```

```
y1 = simplify(ifourier(Y1,w,t))
```

y1 =

$$(3\exp(-2t)(\text{sign}(t) + 1)(\exp(2t) - 1))/2$$

Get y2

Substitute $t - 3$ into t .

$$y2 = \text{subs}(y1, t, t-3)$$

y2 =

$$(3\exp(6 - 2t)(\text{sign}(t - 3) + 1)(\exp(2t - 6) - 1))/2$$


$$y = y1 - y2$$

y =

```
(3*exp(-2*t)*(sign(t) + 1)*(exp(2*t) - 1))/2 - (3*exp(6 - 2*t)*(sign(1 - t)))/2
```

Plot result
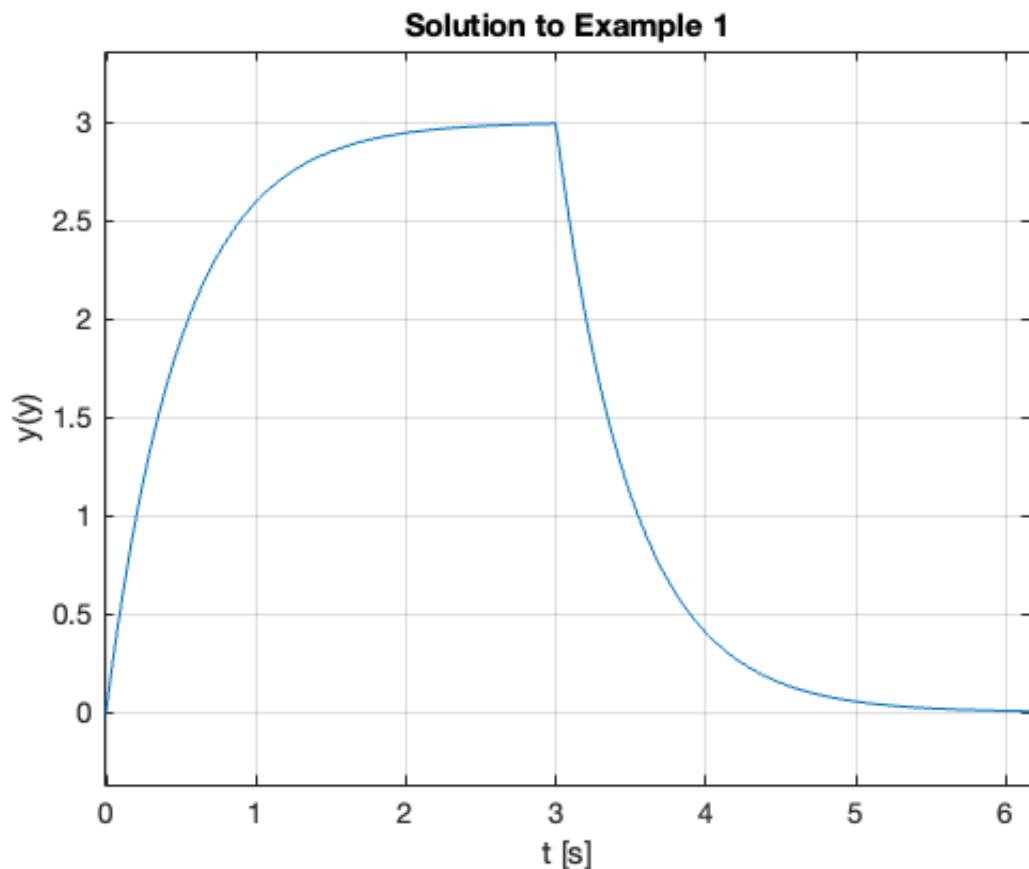
```
ezplot(y)
title('Solution to Example 1')
ylabel('y(t)')
xlabel('t [s]')
grid
```



See [ft3_ex1.m](#)

Result is equivalent to:


$$y = 3*\text{heaviside}(t) - 3*\text{heaviside}(t - 3) + 3*\text{heaviside}(t - 3)*\exp(6 - 2(t-3))$$

Which after gathering terms gives

$$y(t) = 3(1 - 3e^{-2t})u_0(t) - 3(1 - 3e^{-2(t-3)})u_0(t - 3)$$

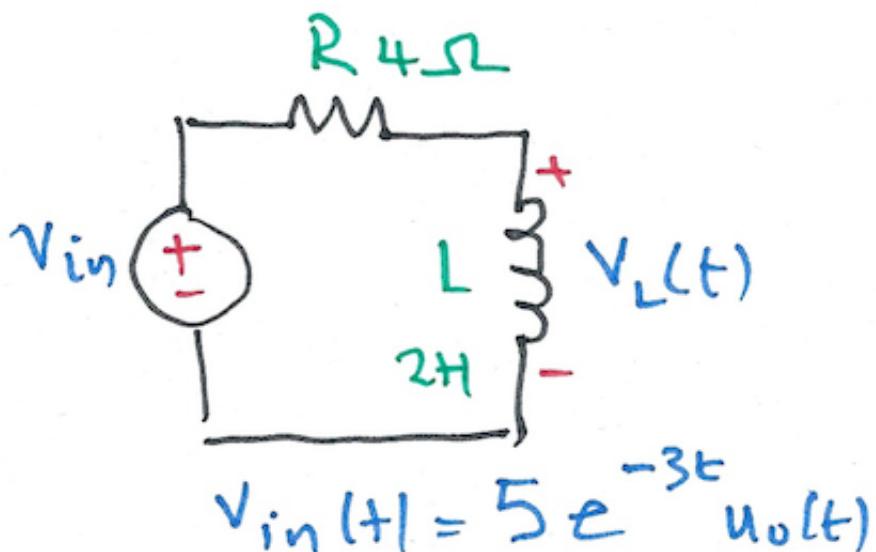Example 2

Karris example 8.9: for the circuit shown below, use the Fourier transform method, and the system function $H(\omega)$ to compute $V_L(t)$. Assume $i_L(0^-) = 0$. Verify the result with Matlab.



Solution of example 2

Matlab verification of example 2

```
syms t w  
H = j*w/(j*w + 2)
```

H =

(w*1i)/(2 + w*1i)

```
Vin = fourier(5*exp(-3*t)*heaviside(t),t,w)
```

Vin =

5/(3 + w*1i)

Vout=simplify(H*Vin)

Vout =

(w*5i)/((2 + w*1i)*(3 + w*1i))


vout = simplify(ifourier(Vout,w,t))

vout =

-(5*exp(-3*t)*(sign(t) + 1)*(2*exp(t) - 3))/2

Plot result
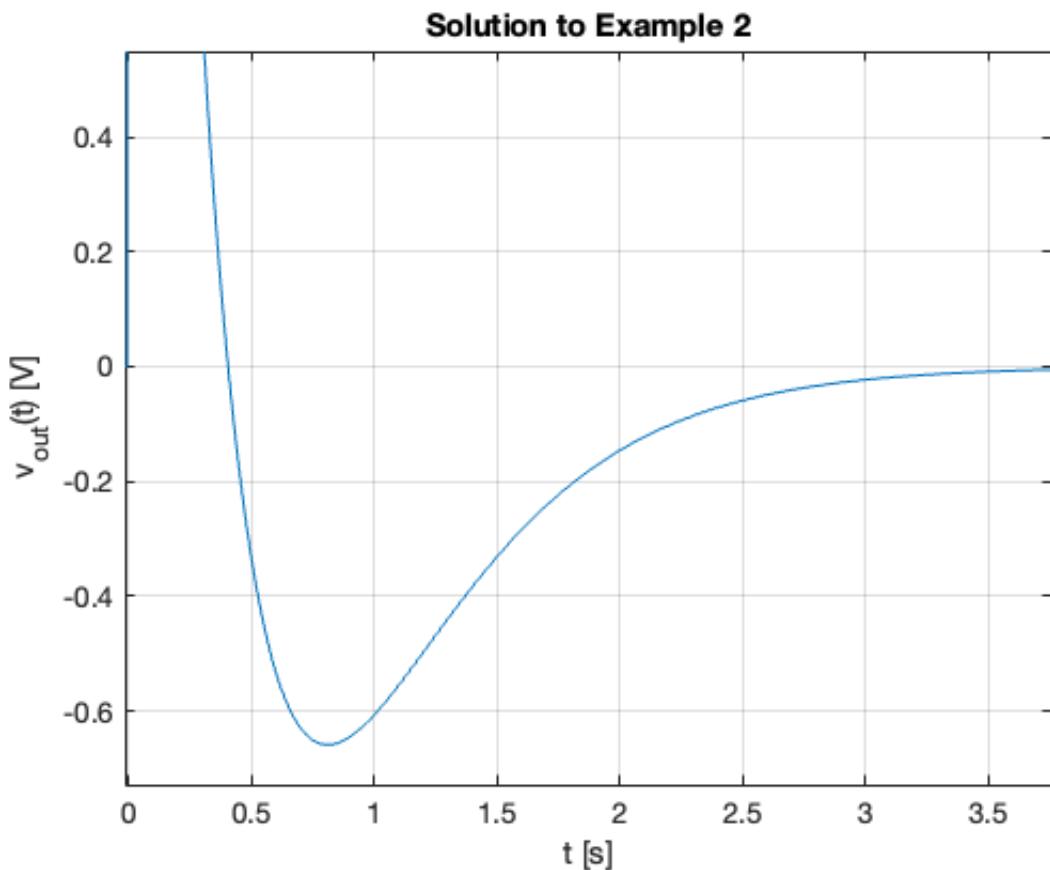
```
ezplot(vout)
title('Solution to Example 2')
ylabel('v_{out}(t) [V]')
xlabel('t [s]')
grid
```



See [ft3_ex2.m](#)

Result is equivalent to:

```
vout = -5*exp(-3*t)*heaviside(t)*(2*exp(t) - 3)
```

Which after gathering terms gives



$$v_{\text{out}} = 5(3e^{-3t} - 2e^{-2t})u_0(t)$$

Example 3

Karris example 8.10: for the linear network shown below, the input-output relationship is:

$$\frac{d}{dt}v_{\text{out}} + 4v_{\text{out}} = 10v_{\text{in}}$$

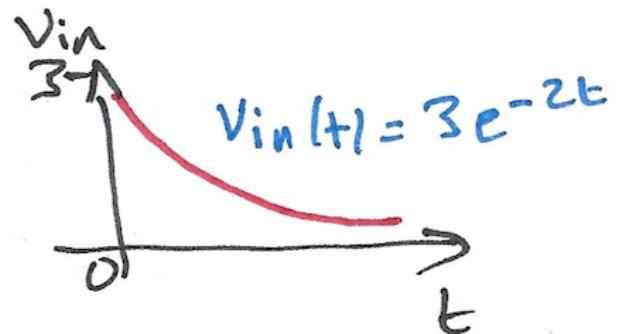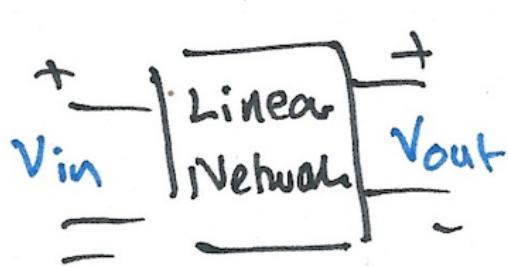where $v_{\text{in}} = 3e^{-2t}$. Use the Fourier transform method, and the system function $H(\omega)$ to compute the output v_{out} . Verify the result with Matlab.



Solution to example 3

Matlab verification of example 3

```
syms t w  
H = 10/(j*w + 4)
```

H =

10/(4 + w*1i)

```
Vin = fourier(3*exp(-2*t)*heaviside(t),t,w)
```

Vin =

$$3/(2 + w*1i)$$

```
Vout=simplify(H*Vin)
```

Vout =

$$30/((2 + w*1i)*(4 + w*1i))$$

```
vout = simplify(ifourier(Vout,w,t))
```

vout =


$$(15*exp(-4*t)*(sign(t) + 1)*(exp(2*t) - 1))/2$$

Plot result

```

ezplot(vout)
title('Solution to Example 3')
ylabel('v_{out}(t) [V]')
xlabel('t [s]')
grid

```

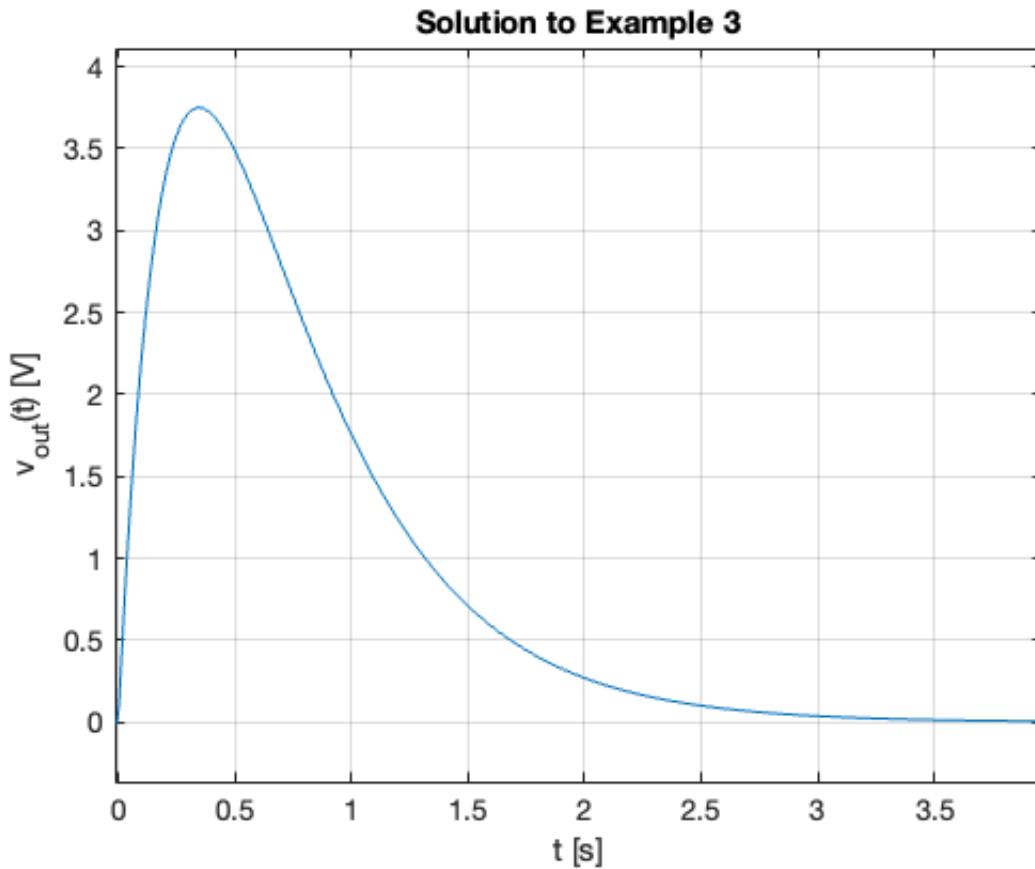

See [ft3_ex3.m](#)

Result is equivalent to:

$$15 \cdot \exp(-4 \cdot t) \cdot \text{heaviside}(t) \cdot (\exp(2 \cdot t) - 1)$$

Which after gathering terms gives


$$v_{\text{out}}(t) = 15 (e^{-2t} - e^{-4t}) u_0(t)$$

Example 4

Karris example 8.11: the voltage across a 1Ω resistor is known to be $V_R(t) = 3e^{-2t}u_0(t)$. Compute the energy dissipated in the resistor for $0 < t < \infty$, and verify the result using Parseval's theorem. Verify the result with Matlab.

Note from [tables of integrals](#)
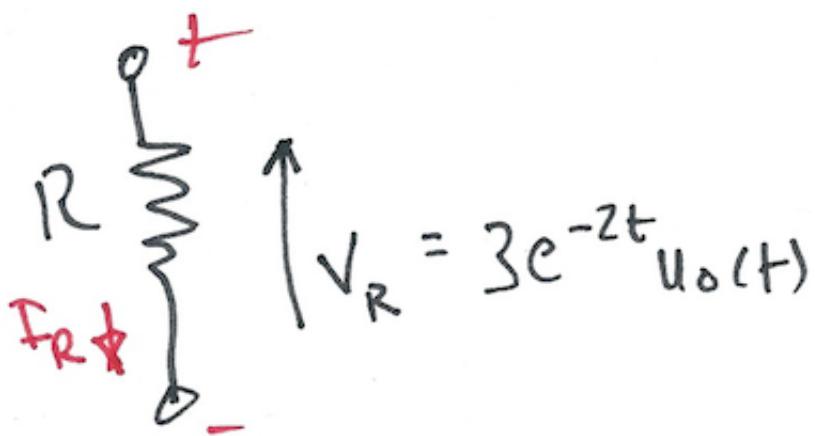
$$\int \frac{1}{a^2 + x^2} dx = \frac{1}{a} \arctan \frac{x}{a} + C.$$



Solution to example 4

Matlab verification of example 4

```
syms t w
```

Calcuate energy from time function

```
Vr = 3*exp(-2*t)*heaviside(t);  
R = 1;  
Pr = Vr^2/R  
Wr = int(Pr,t,0,inf)
```

Pr =

9*exp(-4*t)*heaviside(t)^2

Wr =

9/4

Calculate using Parseval's theorem

$F_w = \text{fourier}(V_r, t, w)$

$F_w =$

$3/(2 + w*1i)$

$F_{w2} = \text{simplify}(\text{abs}(F_w)^2)$

$F_{w2} =$

9/abs(2 + w*1i)^2

Wr=2/(2*pi)*int(Fw2,w,0,inf)

Wr =

(51607450253003931*pi)/72057594037927936

See [ft3_ex4.m](#)

Solutions

- Example 1: [ft3-ex1.pdf](#)
- Example 2: [ft3-ex2.pdf](#)
- Example 3: [ft3-ex3.pdf](#)
- Example 3: [ft3-ex4.pdf](#)

Previous

< [4.2: Fourier transforms of commonly occurring signals](#)

Next

[Introduction to Filters](#) >